

Name :- Chandrawanesh Mangesh Shivaji

Roll No :- 1801CS16.

Date :- 16/04/2020.

Sign :-

Chandraw.

CS226 - Switching Theory Lab - 9

Q.1) 4-bit synchronous counter

(a) Using S-R flipflop :

4 flip-flops required to hold states

clock signal controls when flip-flop memory can change.

Present state				Next state				Flip-flop Input							
C_4	C_3	C_2	C_1	N_4	N_3	N_2	N_1	S_4	R_4	S_3	R_3	S_2	R_2	S_1	R_1
0	0	0	0	0	0	0	1	0	X	0	X	0	X	1	0
0	0	0	1	0	0	1	0	0	X	0	X	0	X	0	1
0	0	1	0	0	0	1	1	0	X	0	X	0	X	1	0
0	0	1	1	0	1	0	0	0	X	1	0	0	1	0	1
0	1	0	0	0	1	0	1	0	X	X	0	0	X	1	0
0	1	0	1	0	1	1	0	0	X	X	0	1	0	0	1
0	1	1	0	0	1	1	1	0	X	X	0	X	0	1	0
0	1	1	1	1	0	0	0	1	0	0	1	0	1	0	1
1	0	0	0	1	0	0	1	X	0	0	X	0	X	1	0
1	0	0	1	1	0	1	0	X	0	0	X	1	0	0	1
1	0	1	0	1	0	1	1	X	0	0	X	X	0	1	0
1	0	1	1	1	1	0	0	X	0	1	0	0	1	0	1
1	1	0	0	1	1	0	1	X	0	X	0	0	X	1	0
1	1	0	1	1	1	1	0	X	0	X	0	1	0	0	1
1	1	1	0	1	1	1	1	X	0	X	0	X	0	1	0
1	1	1	1	0	0	0	0	0	1	0	1	0	1	0	1



Excitation Table

Q	$Q(\text{next})$	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

$C_4 \backslash C_2$	00	01	11	10
00	1	0	0	1
01	1	0	0	1
11	1	0	0	1
10	1	0	0	1

$$S_1 = C_1^1$$

$C_4 \backslash C_2$	00	01	11	10
00	0	1	1	0
01	0	1	1	0
11	0	1	1	0
10	0	1	1	0

$$R_1 = C_1$$

$C_4 \backslash C_2$	00	01	11	10
00	0	1	0	X
01	0	1	0	X
11	0	1	0	X
10	0	1	0	X

$$S_2 = C_1 C_2^1$$

$C_4 \backslash C_2$	00	01	11	10
00	X	0	1	0
01	X	0	1	0
11	X	0	1	0
10	X	0	1	0

$$R_2 = C_1 C_2$$

$C_4 \backslash C_2$	00	01	11	10
00	0	0	1	0
01	X	X	0	X
11	X	X	0	X
10	0	0	1	0

$$S_3 = C_1 C_2 C_3^1$$

$C_4 \backslash C_2$	00	01	11	10
00	X	X	0	X
01	0	0	1	0
11	0	0	1	0
10	X	X	0	X

$$R_3 = C_1 C_2 C_3$$

$C_4 \backslash C_2$	00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	X	X	0	X
10	X	X	X	X

$$S_4 = C_1 C_2 C_3 C_4^1$$

$C_4 \backslash C_2$	00	01	11	10
00	X	X	X	X
01	X	X	0	X
11	0	0	1	0
10	0	0	0	0

$$R_4 = C_1 C_2 C_3 C_4$$

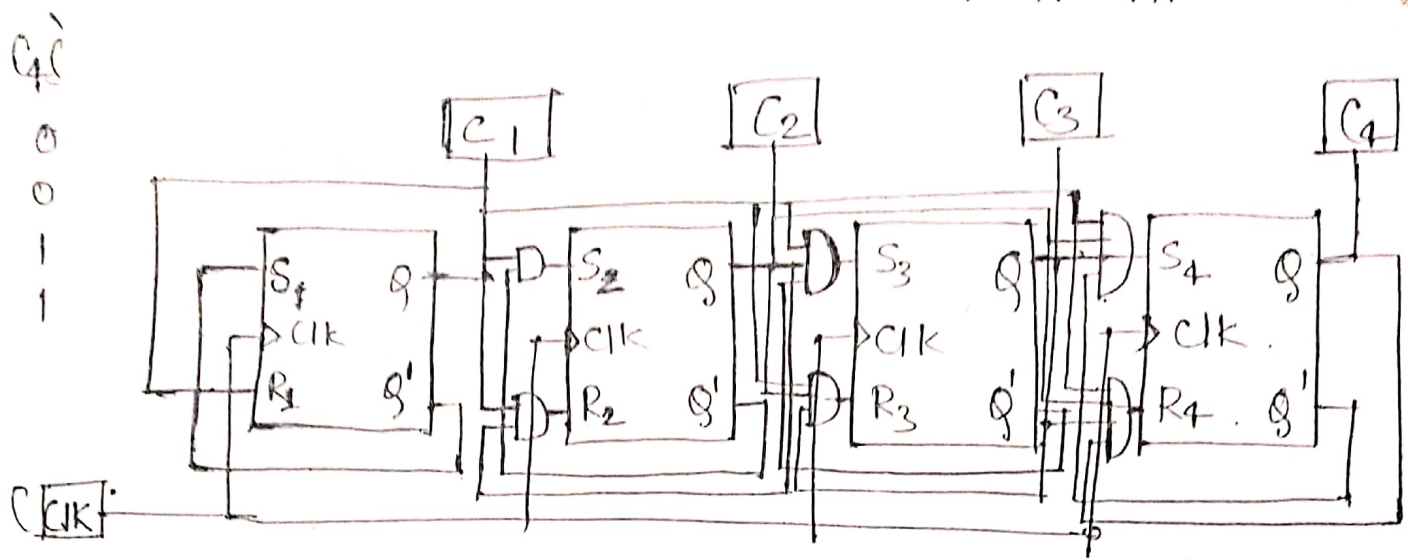


Fig. 4-bit RS counter (synchronous).

$$S_1 = C_1' \quad R_1 = C_1 \quad S_2 = C_1 C_2' \quad R_2 = C_1 C_2 \quad S_3 = C_1 C_2 C_3' \quad R_3 = C_1 C_2 C_3$$


$$S_4 = C_1 C_2 C_3 C_4' \quad R_4 = C_1 C_2 C_3 C_4$$

(b) Using J-K flipflop.

4-flipflops req. to hold states.

clock signal changes when flip-flop memory can change.

Q	Q _{next}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

 

Excitation Table.

Present state				Next State				Flip-flop Inputs			
C_4	C_3	C_2	C_1	N_4	N_3	N_2	N_1	$J_4 K_4$	$J_3 K_3$	$J_2 K_2$	$J_1 K_1$
0	0	0	0	0	0	0	1	0 X	0 X	0 X	1 X
0	0	0	1	0	0	1	0	0 X	0 X	1 X	X 1
0	0	1	0	0	0	1	1	0 X	0 X	X 0	1 X
0	0	1	1	0	1	0	0	0 X	1 X	X 1	X 1
0	1	0	0	0	1	0	1	0 X	X 0	0 X	1 X
0	1	0	1	0	1	1	0	0 X	X 0	1 X	X 1
0	1	1	0	0	1	1	1	0 X	X 0	X 0	1 X
0	1	1	1	1	0	0	0	1 X	X 1	X 1	X 1
1	0	0	0	1	0	0	1	X 0	0 X	0 X	1 X
1	0	0	1	1	0	1	0	X 0	0 X	1 X	X 1
1	0	1	0	1	0	1	1	X 0	0 X	X 0	1 X
1	0	1	1	1	1	0	0	X 0	1 X	X 1	X 1
1	1	0	0	1	1	0	1	X 0	X 0	0 X	1 X
1	1	0	1	1	1	1	0	X 0	X 0	1 X	X 1
1	1	1	0	1	1	1	1	X 0	X 0	X 0	1 X
1	1	1	1	0	0	0	0	X 1	X 1	X 1	X 1

$C_4 \backslash C_3$	00	01	11	10
00	1	X	X	1
01	1	X	X	1
11	1	X	X	1
10	1	X	X	1

$$J_1 = 1$$

$C_4 \backslash C_3$	00	01	11	10
00	X	1	1	X
01	X	1	X	X
11	X	1	1	X
10	X	1	1	X

$$K_1 = 1$$

Q_3/Q_2 00 01 10 11

00	0	1	X	X
01	0	1	X	X
10	0	1	X	X
11	0	1	X	X

$$J_2 = C_1$$

Q_3/Q_2 00 01 11 10

00	X	X	1	0
01	X	X	1	0
11	X	X	1	0
10	X	X	1	0

$$K_2 = C_1$$

Q_3/Q_2 00 01 11 10

00	0	0	1	0
01	X	X	X	X
11	X	X	X	X
10	0	0	1	0

$$J_3 = Q_2$$

Q_3/Q_2 00 01 11 10

00	X	X	X	X
01	0	0	1	0
11	0	0	1	0
10	X	X	X	X

$$K_3 = Q_2$$

Q_3/Q_2	00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	X	X	X	X
10	X	X	X	X

$$J_4 = Q_2 Q_3$$

Q_3/Q_2	00	01	11	10
00	X	X	X	X
01	X	X	X	X
11	0	0	1	0
10	0	0	0	0

$$K_4 = Q_2 Q_3$$

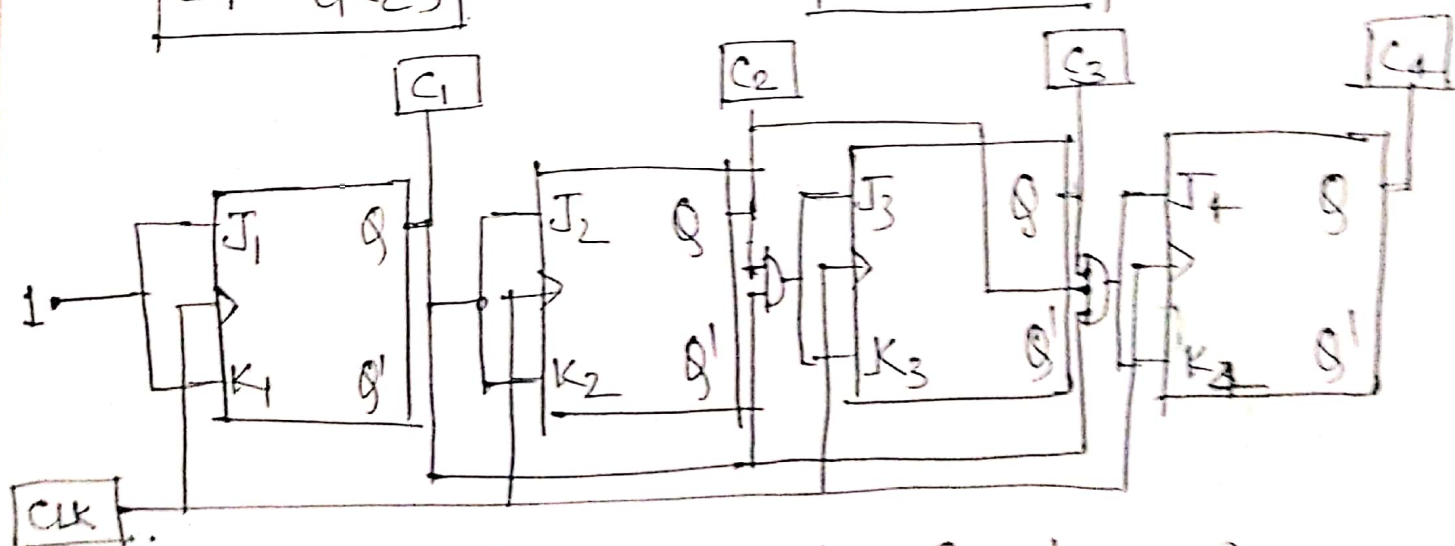


Fig. 4-bit J-K Counter (Synchronous)

(c) Using T-flipflop: 4 flipflop. 1 rising edge of clock pulse
memory state changes



Fig. T-flipflop

Q	Q(next)	T
0	0	0
0	1	1
1	0	1
1	1	0

Excitation Table

Present State				Next State				Flip-flop Inputs			
C ₄	C ₃	C ₂	C ₁	N ₄	N ₃	N ₂	N ₁	T ₄	T ₃	T ₂	T ₁
0	0	0	0	0	0	0	1	0	0	0	1
0	0	0	1	0	0	1	0	0	0	1	1
0	0	1	0	0	0	1	1	0	0	0	1
0	0	1	1	0	1	0	0	0	1	1	1
0	1	0	0	0	1	0	1	0	0	0	1
0	1	0	1	0	1	1	0	0	0	0	1
0	1	1	0	0	1	1	1	0	1	1	1
0	1	1	1	1	0	0	0	1	1	0	1
1	0	0	0	1	0	0	1	0	0	0	1
1	0	0	1	1	0	1	0	0	0	1	1
1	0	1	0	1	0	1	1	0	0	0	1
1	0	1	1	1	1	0	0	0	1	1	1
1	1	0	0	1	1	0	1	0	0	1	1
1	1	0	1	1	1	1	0	0	0	0	1
1	1	1	0	1	1	1	1	0	0	0	1
1	1	1	1	0	0	0	0	1	1	1	1

$$\begin{array}{c|cccc} C_4 \backslash C_3 \backslash C_2 \backslash C_1 & 00 & 01 & 11 & 10 \\ \hline 00 & 1 & 1 & 1 & 1 \\ 01 & 1 & 1 & 1 & 1 \\ 11 & 1 & 1 & 1 & 1 \\ 10 & 1 & 1 & 1 & 1 \end{array}$$

$$T_1 = 1$$

$$\begin{array}{c|cc|cc} C_4 \backslash C_3 \backslash C_2 \backslash C_1 & 00 & 01 & 11 & 10 \\ \hline 00 & 0 & 1 & 1 & 0 \\ 01 & 0 & 1 & 1 & 0 \\ 11 & 0 & 1 & 1 & 0 \\ 10 & 0 & 1 & 1 & 0 \end{array}$$

$$T_2 = C_1$$

$$\begin{array}{c|ccc|c} C_4 \backslash C_3 \backslash C_2 \backslash C_1 & 00 & 01 & 11 & 10 \\ \hline 00 & 0 & 0 & 1 & 0 \\ 01 & 0 & 0 & 1 & 0 \\ 11 & 0 & 0 & 1 & 0 \\ 10 & 0 & 0 & 1 & 0 \end{array}$$

$$T_3 = C_1 C_2$$

$$\begin{array}{c|ccc|c} C_4 \backslash C_3 \backslash C_2 \backslash C_1 & 00 & 01 & 11 & 10 \\ \hline 00 & 0 & 0 & 0 & 0 \\ 01 & 0 & 0 & 1 & 0 \\ 11 & 0 & 0 & 1 & 0 \\ 10 & 0 & 0 & 0 & 0 \end{array}$$

$$T_4 = C_1 C_2 C_3$$


 


Fig. 4-bit T counter (synchronous)

(d) Using D-flipflop . 4 flipflops req .

 

Excitation Table .

Q	Q _{next}	D
0	0	0
0	1	1
1	0	0
1	1	1

Present State				Next State				flip-flop inputs			
C_4	C_3	C_2	C_1	N_4	N_3	N_2	N_1	D_4	D_3	D_2	D_1
0	0	0	0	0	0	0	1	0	0	0	1
0	0	0	1	0	0	1	0	0	0	1	0
0	0	1	0	0	0	1	1	0	0	1	1
0	0	1	1	0	1	0	0	0	1	0	0
0	1	0	0	0	1	0	1	0	1	0	1
0	1	0	1	0	1	1	0	0	1	1	0
0	1	1	0	0	1	1	1	0	1	1	1
0	1	1	1	0	1	0	0	1	0	0	0
1	0	0	0	1	0	0	1	1	0	0	1
1	0	0	1	1	0	1	0	1	0	1	0
1	0	1	0	1	0	1	1	1	0	1	1
1	0	1	1	1	1	0	0	1	1	0	0
1	1	0	0	1	1	0	1	1	1	0	1
1	1	0	1	1	1	1	0	1	1	1	0
1	1	1	0	1	1	1	1	1	1	1	1
1	1	1	1	0	0	0	0	0	0	0	0

$C_3 \backslash C_2$	00	01	11	10
00	1	0	0	1
01	1	0	0	1
11	1	0	0	1
10	1	0	0	1

$$D_1 = C_1'$$

$C_3 \backslash C_2$	00	01	11	10
00	0	1	0	1
01	0	1	0	1
11	0	1	0	1
10	0	1	0	1

$$D_2 = C_1 C_2' + C_2 C_1' = C_1 \oplus C_2$$

$$\begin{array}{c|ccc} C_4 \backslash C_3 & 00 & 01 & 11 & 10 \\ \hline 00 & 0 & 0 & 1 & 0 \\ 01 & 1 & 1 & 0 & 1 \\ 11 & 1 & 1 & 0 & 1 \\ 10 & 0 & 0 & 1 & 0 \end{array}$$

$$\begin{array}{c|ccc} C_4 \backslash C_3 & 00 & 01 & 11 & 10 \\ \hline 00 & 0 & 0 & 0 & 0 \\ 01 & 0 & 0 & 1 & 0 \\ 11 & 1 & 1 & 0 & 1 \\ 10 & 1 & 1 & 1 & 1 \end{array}$$

$$D_3 = C_3 C_2' + C_3 C_1' + C_1 C_2 C_3'$$

$$D_3 = (C_1 C_2) \oplus C_3$$

$$D_4 = C_4 C_3' + C_4 C_2' + C_4 C_1' + C_4' C_1 C_2 C_3$$

$$= C_4 (C_1' + C_2' + C_3') + C_4' C_1 C_2 C_3$$

$$= C_4 (C_1 C_2 C_3)' + (C_1 C_2 C_3) C_4'$$

$$D_4 = (C_1 C_2 C_3) \oplus C_4$$

 


Fig. 4 bit D counter (synchronous)

Q.2) Design a register file (16x16) with two read ports and one write port. Perform read and write operation and understand the operation of register file.

D \Rightarrow IP of register
en \Rightarrow Enabler.

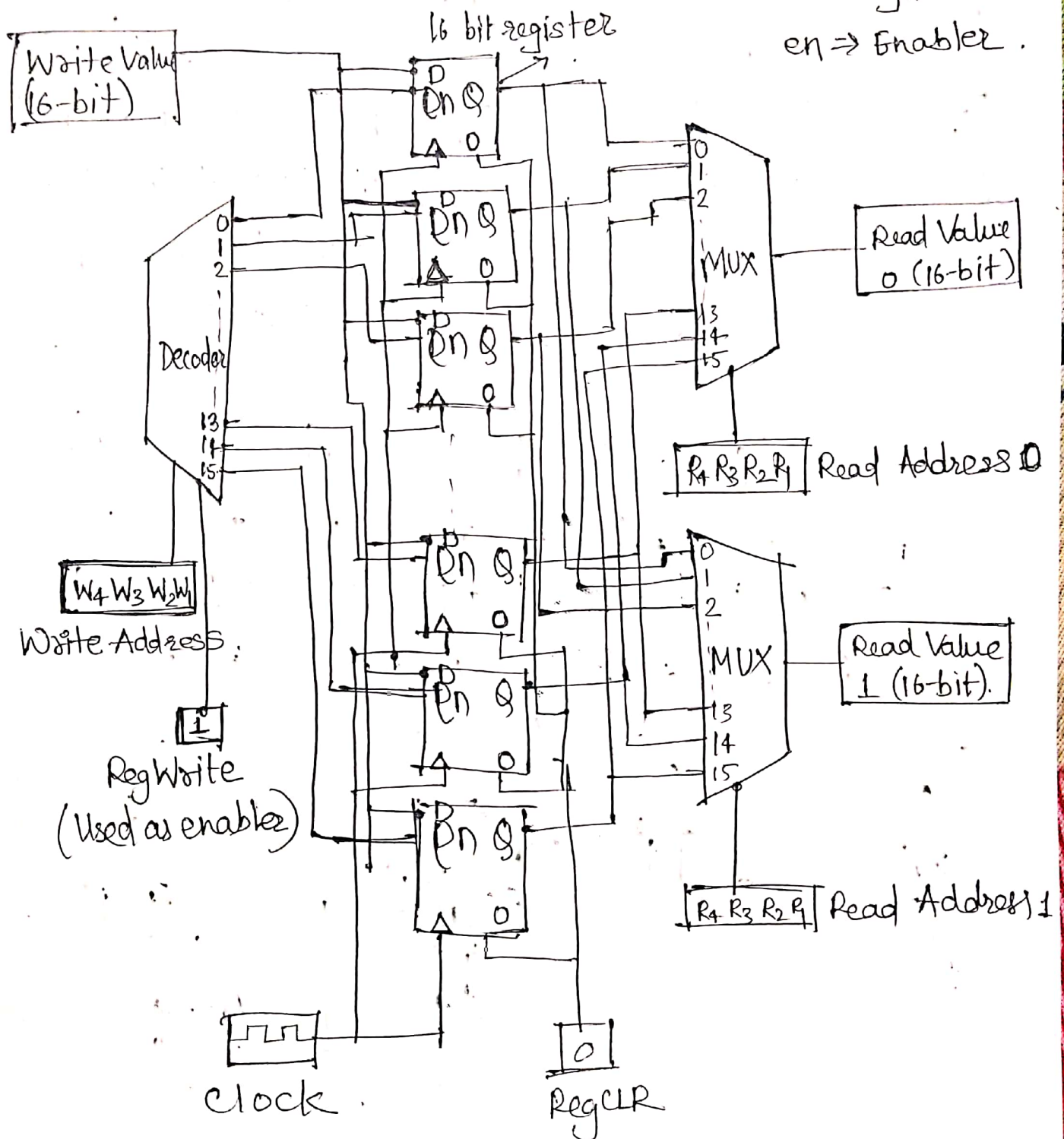


Fig. 16x16. Register file with two read ports and one write port.


Write Operation :-

- ① Put the value to be written in Write Value.
- ② Mention Write Address corresponding to the register where you want to store the value.
- ③ Set RegWrite (enabler) for Decoder to 1.
- ④ Generate a clock pulse. At the rising edge, value gets stored (written).

Read Operation :-

- ① Mention Read Address corresponding to the register, where you want to read value from.
- ② Generate a clock pulse, at the rising edge of which value is read and displayed.

Q.3) Combine register file and ALU

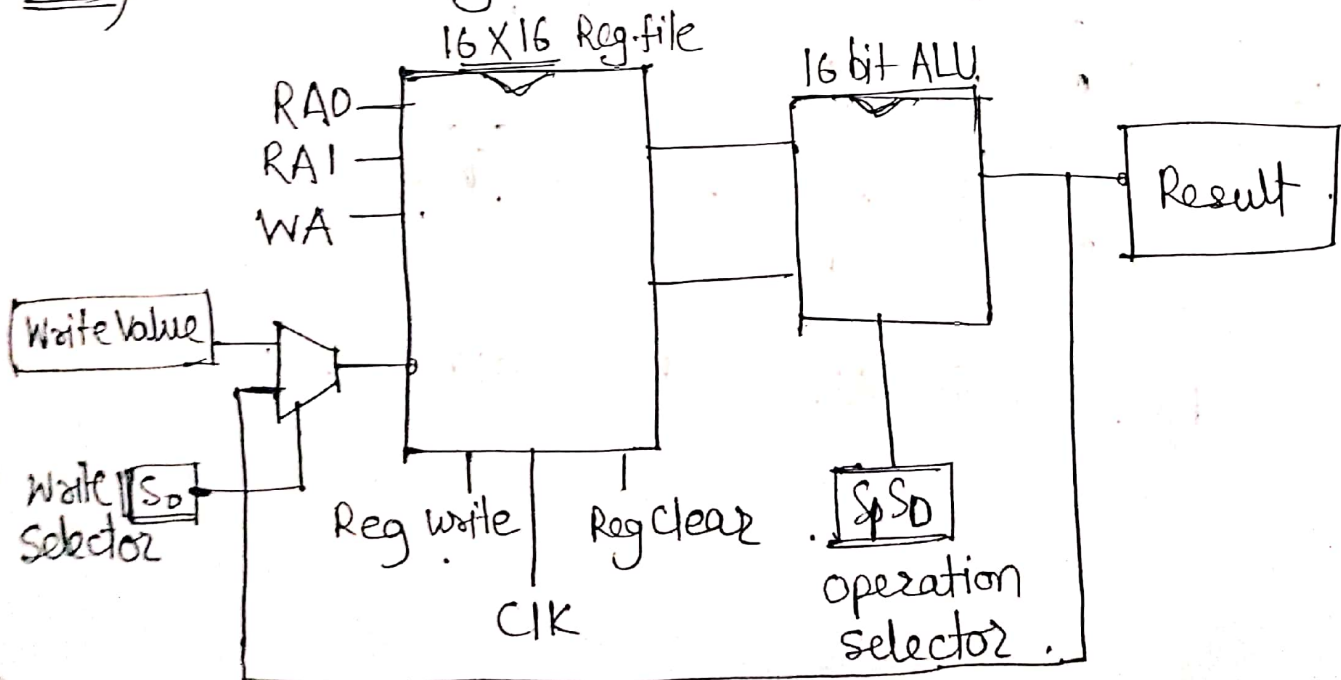

Write Selector

S_0	Operation
0	Writes Input Value to Write Addr
1	Writes Result to Write Addr

Operation Selector

S_0	S_1	Operation
0	0	Addition
0	1	Subtraction
1	0	Bitwise AND
1	1	Bitwise OR

16-bit ALU

16-bit Reg. file \Rightarrow same as question 2.
16-bit ALU.

 


Fig. 16-bit ALU. (4 operations)

Write 1, 2, ..., 10 data to registers (1 to 10) and compute sum.

→ Steps

Write Selector = 0; RegWrite = 1. for every read and write operation we have to give a clock pulse.

Write Address	Write Value
0001	0001
0010	0010
0011	0011
0100	0100
0101	0101
0110	0110
0111	0111
1000	1000
1001	1001
1010	1001

Write Selector = 1.

Read Ad 0	Read Ad 1	Result (in decimal).
0000.	0001.	1 → write it
1011	0010.	3 to 1011
1011	0011	6 —//—
1011	0100	10 —//—
1011	0101	15 —//—
1011	0110	21 —//—
1011	0111	28 —//—
1011	1000	36 —//—
1011	1001	45 —//—
1011	1010	55 —//—

final answer