
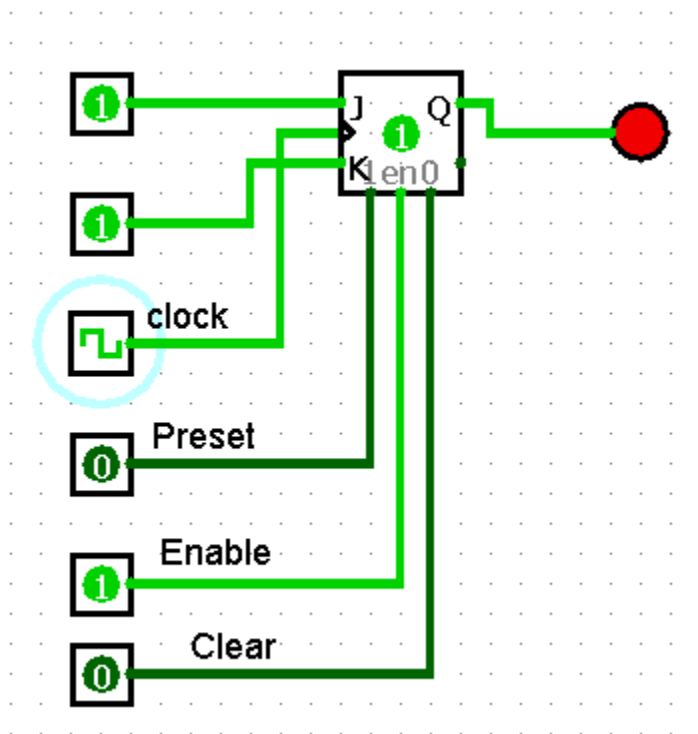


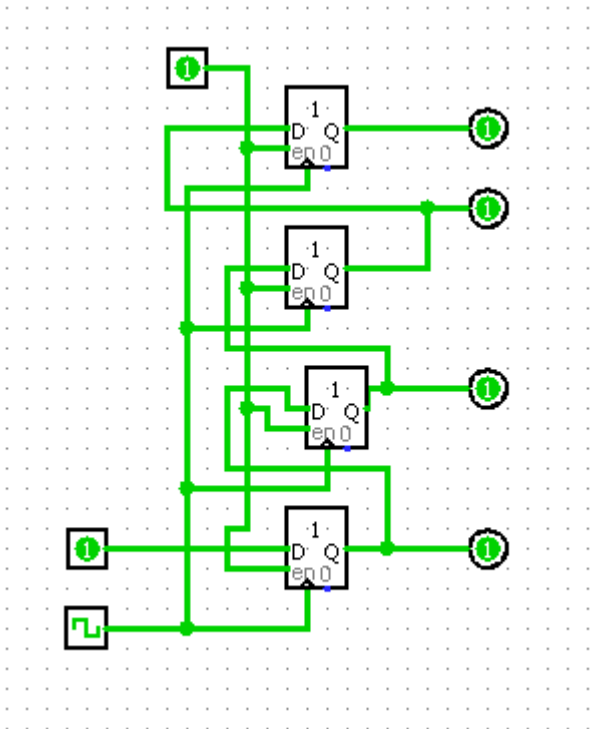Q0: Study basic sequential elements SR, J-K ,T and D flip flops.


Eg. J-K example is shown here. Test all possible input combinations for each of the memory elements.




Q1: Simulate a 8 bit shift register using logic-sim. A 4 bit shift register design is shown.



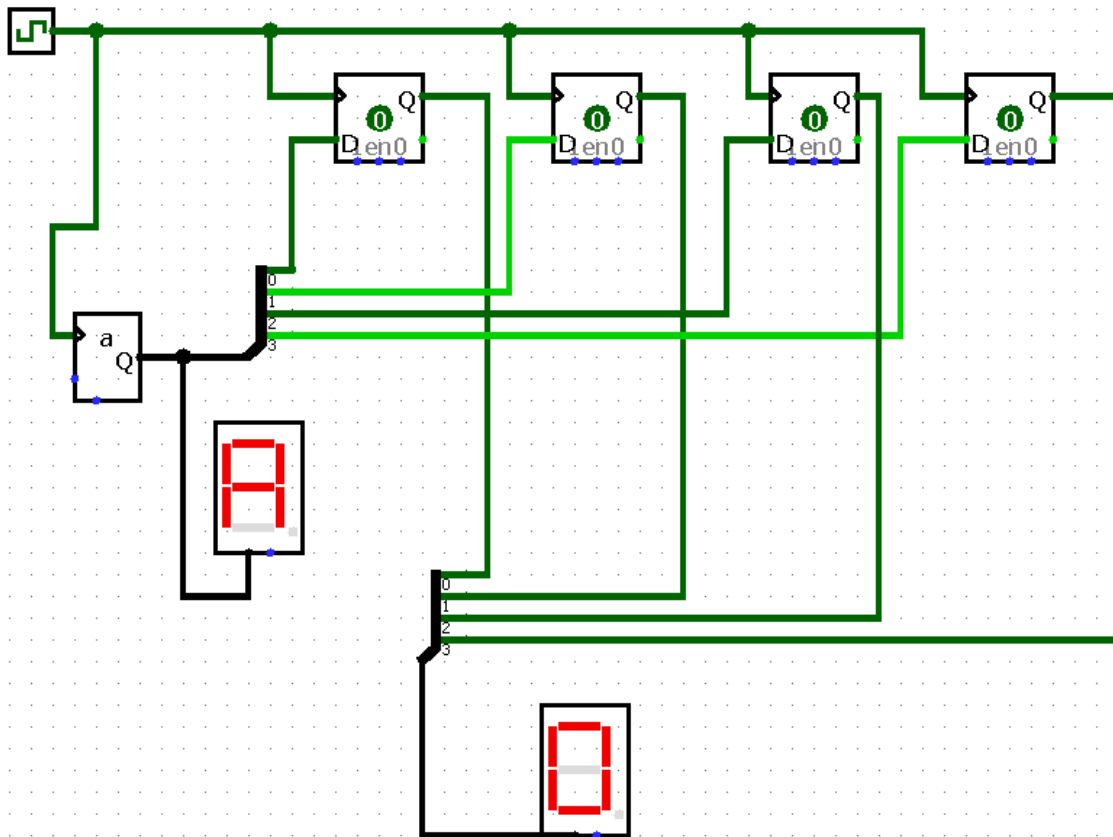**Q2:** Simulate a 4 bit parallel in Parallel out(PIPO) register. Design a 4 bit parallel in Parallel out(PIPO) register.



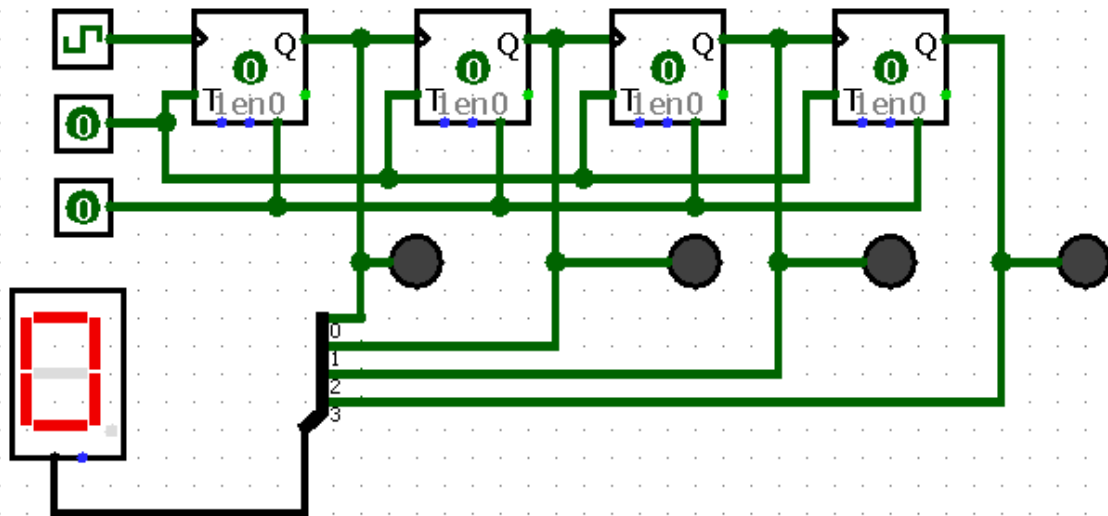
**Q3:** Simulate a 4 bit counter using T flip flops. Design a 6 bit counter using T flip flops




Q4: Simulate the multi-function Shift register using logic-sim. Design an 8 bit version.

### Functions:

s1	s0	Operation
0	0	Maintain present value
0	1	Parallel load
1	0	Shift right
1	1	(unused - let's load 0s)

 


(a)

 

(b)

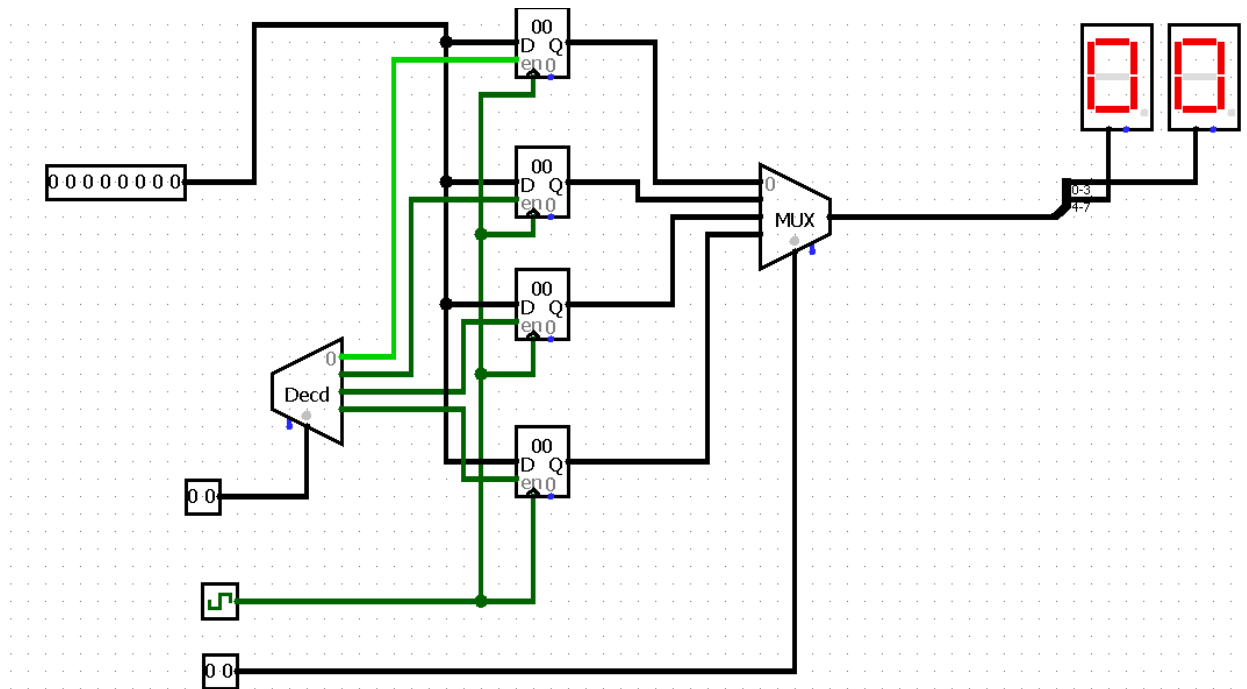Q5: Here a 4x8 register file is shown. Design a 16x16 register file ( include register file enable)



**Logic-sim simulation submission should be individual.** Course work submission through  
 Email: [cs225.iitp@gmail.com](mailto:cs225.iitp@gmail.com)  
 (use email subject Lab8\_Logicsim\_your roll number).

Include a detailed word document or pdf with answers to each of the questions along with .circ file.

(submit a single zip file-doc+ \*.circ s). Submission deadline 7<sup>th</sup> April 5 PM.

# Meeting Information

Meeting Topic:	jimson jimson's Personal Room
Location:	<a href="https://iitpatna.webex.com/iitpa...">https://iitpatna.webex.com/iitpa...</a>
Meeting number:	577 377 383
India Toll (Delhi):	+91-11-6480-0114
India Toll (Hyderabad):	+91-40-6480-0114
> Global call-in numbers	
Access code:	577 377 383