

Name :- Chandrawanshi Mangesh Shivaji

Roll No. :- 1801CS16

Sign :- Chandrawanshi

Date :- 23/04/2020

CS226 - Switching Theory Lab-10

Q.1) Design a - twobit counter with following specs .


C_0	C_1	Operation
0	0	Stop Counting
0	1	Count up by one
1	0	Count down by one
1	1	Count by two

State diagram

Total no. of states = 4 .

00, 01, 10, 11 .

No. of flipflops required = 2 .

 

On each arrow, in the direction of arrow
Inputs C_0, C_1 are mentioned respectively .

2 Implementation using D-Flipflop

Inputs		Current State		Next State		Flipflop Inputs	
C_0	C_1	S_0	S_1	N_0	N_1	D_0	D_1
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0
0	0	1	0	1	0	1	0
0	0	1	1	0	0	0	0
0	1	0	0	0	1	0	1
0	1	0	1	1	0	1	0
0	1	1	0	1	1	1	1
0	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1
1	0	0	1	0	0	0	0
1	0	1	0	0	1	0	1
1	0	1	1	1	0	1	0
1	1	0	0	0	0	0	0
1	1	0	1	1	0	1	1
1	1	1	0	0	0	0	0
1	1	1	1	0	1	0	1

$C_0 \backslash S_1 S_0$	00	01	11	10
00	0	0	1	1
01	0	1	0	1
11	1	1	0	0
10	1	0	1	0

$$D_1 = C_0 \bar{S}_0 \bar{S}_1 + C_1 \bar{S}_0 \bar{S}_1 + \bar{C}_1 S_0 S_1 + \bar{C}_0 \bar{S}_0 S_1$$

$C_0 \backslash S_1 S_0$	00	01	11	10
00	0	1	1	0
01	1	0	0	1
11	0	1	1	0
10	1	0	0	1

$$D_0 = S_0 (\bar{C}_1 \bar{C}_0 + C_1 C_0) + \bar{S}_0 (C_1 \oplus C_0)$$

 


Fig. 2-bit counter using D flipflops.

(b) Implementation using T-flipflop.

Operation		Current state		Next state		Flipflop Inputs	
C_0	Q	S_1	S_0	N_1	N_0	T_1	T_0
0	0	0	0	0	0	0	0
0	0	0	1	0	1	0	0
0	0	1	0	1	0	0	0
0	0	1	1	1	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	1	0	1	1
0	1	1	0	1	1	0	1
0	1	1	1	0	0	1	1
1	0	0	0	1	1	1	1
1	0	0	1	0	0	0	1
1	0	1	0	0	1	1	1
1	0	1	1	1	0	0	1
1	1	0	0	1	0	1	0
1	1	0	1	1	1	1	0
1	1	1	0	0	0	1	0
1	1	1	1	0	1	1	0

$S_1 S_0$	00	01	11	10
$C_0 C_1$	00	00	00	00
01	0	1	1	0
11	1	1	1	1
10	1	0	0	1

$$T_1 = S_0 C_1 + \overline{S_0} C_0$$

$S_1 S_0$	00	01	11	10
$C_0 C_1$	00	00	00	00
01	1	1	1	1
11	0	0	0	0
10	1	1	1	1

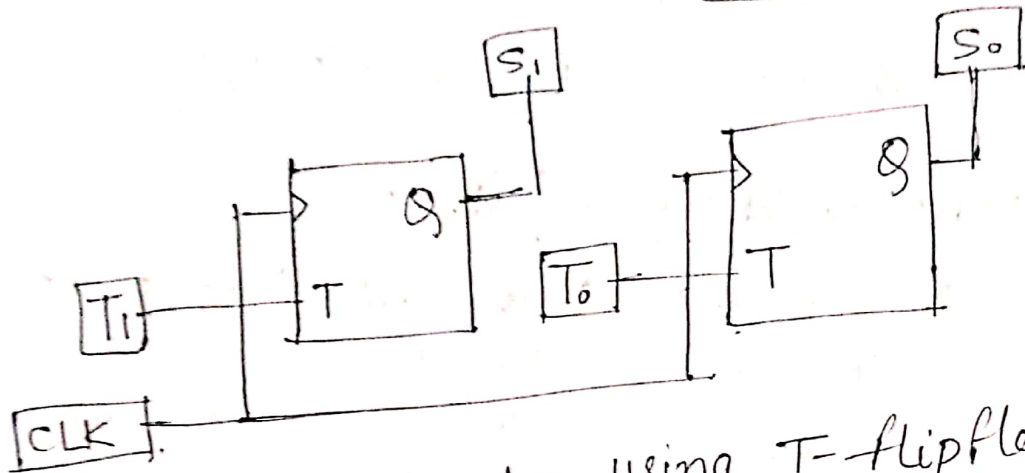
$$T_0 = C_0 \oplus C_1$$


Fig. 2-bit counter using T-flipflop.

(c) Implementation using SR flipflop.

 


Fig. 2-bit counter using SR flipflop.

Inputs		Current state		Next state		Flipflop Inputs			
C_0	C_1	S_1	S_0	N_1	N_0	S_1	R_1	S_0	R_0
0	0	0	0	0	0	0	X	0	X
0	0	0	1	0	1	0	X	X	0
0	0	1	0	1	0	X	0	0	X
0	0	1	1	1	1	X	0	X	0
0	1	0	0	0	1	0	X	1	0
0	1	0	1	1	0	1	0	0	1
0	1	1	0	1	1	X	0	1	0
0	1	1	1	0	0	0	1	0	1
1	0	0	0	1	1	1	0	1	0
1	0	0	1	0	0	0	X	0	1
1	0	1	0	0	1	0	1	1	0
1	0	1	1	1	0	X	0	0	1
1	1	0	0	1	0	1	0	0	X
1	1	0	1	1	1	1	0	X	0
1	1	1	0	0	0	0	1	0	X
1	1	1	1	0	1	0	1	X	0

C_0	C_1	S_1	S_0
00	00	01	11
00	00	0	X
01	0	1	0
11	1	1	0
10	1	0	X

$$S_1 = C_0 \bar{S}_1 \bar{S}_0 + C_1 \bar{S}_1 \bar{S}_0$$

C_0	C_1	S_1	S_0
00	00	01	11
00	00	X	X
01	0	X	0
11	1	0	0
10	1	0	X

$$R_1 = C_1 S_1 S_0 + C_0 S_1 S_0$$

C_0	C_1	S_1	S_0
00	00	01	11
00	00	0	X
01	0	1	0
11	1	1	0
10	1	0	0

$$S_0 = \bar{C}_0 \bar{C}_1 \bar{S}_1 \bar{S}_0 + C_0 \bar{C}_1 \bar{S}_1 \bar{S}_0$$

C_0	C_1	S_1	S_0
00	00	01	11
00	00	X	0
01	0	0	1
11	1	X	0
10	1	0	0

$$R_0 = \bar{C}_0 \bar{C}_1 S_1 S_0 + C_0 \bar{C}_1 S_1 S_0$$

(d) Implementation using JK flipflop

Inputs	Current State		Next State		Flipflop Inputs			
$C_0 C_1$	S_1	S_0	N_1	N_0	J_1	K_1	J_0	K_0
0 0	0	0	0	0	0	X	0	X
0 0	0	1	0	1	0	X	X	0
0 0	1	0	1	0	X	0	0	X
0 0	1	1	1	1	X	0	X	0
0 1	0	0	0	1	0	X	1	X
0 1	0	1	1	0	1	X	X	1
0 1	1	0	1	1	X	0	1	X
0 1	1	1	0	0	X	1	X	1
1 0	0	0	1	1	1	X	1	X
1 0	0	1	0	0	0	X	X	1
1 0	1	0	0	1	X	1	1	X
1 0	1	1	1	0	X	0	X	1
1 1	0	0	1	0	1	X	0	X
1 1	0	1	1	1	1	X	X	0
1 1	1	0	0	0	X	1	0	X
1 1	1	1	0	1	X	1	X	0

$\begin{array}{c|cccc} C_1 \backslash S_0 & 00 & 01 & 11 & 10 \\ \hline 00 & 0 & 0 & X & X \\ 01 & 0 & 1 & X & X \\ 11 & 1 & 1 & X & X \\ 10 & 1 & 0 & X & X \end{array}$
 $J_1 = C_0 \bar{S}_0 + C_1 S_0$

$\begin{array}{c|cccc} C_1 \backslash S_0 & 00 & 01 & 11 & 10 \\ \hline 00 & 0 & X & X & 0 \\ 01 & 1 & X & X & 1 \\ 11 & 0 & X & X & 0 \\ 10 & 1 & X & X & 1 \end{array}$
 $J_0 = \bar{C}_0 C_1 + C_0 \bar{C}_1 = C_1 \oplus C_0$

$\begin{array}{c|cccc} C_1 \backslash S_0 & 00 & 01 & 11 & 10 \\ \hline 00 & X & X & 0 & 0 \\ 01 & X & X & 1 & 0 \\ 11 & X & X & 1 & 1 \\ 10 & X & X & 0 & 1 \end{array}$
 $K_1 = C_1 S_0 + C_0 \bar{S}_0$

$\begin{array}{c|cccc} C_1 \backslash S_0 & 00 & 01 & 11 & 10 \\ \hline 00 & X & 0 & 0 & X \\ 01 & X & 1 & 1 & X \\ 11 & X & 0 & 0 & X \\ 10 & X & 1 & 1 & X \end{array}$
 $K_0 = C_1 \oplus C_0$

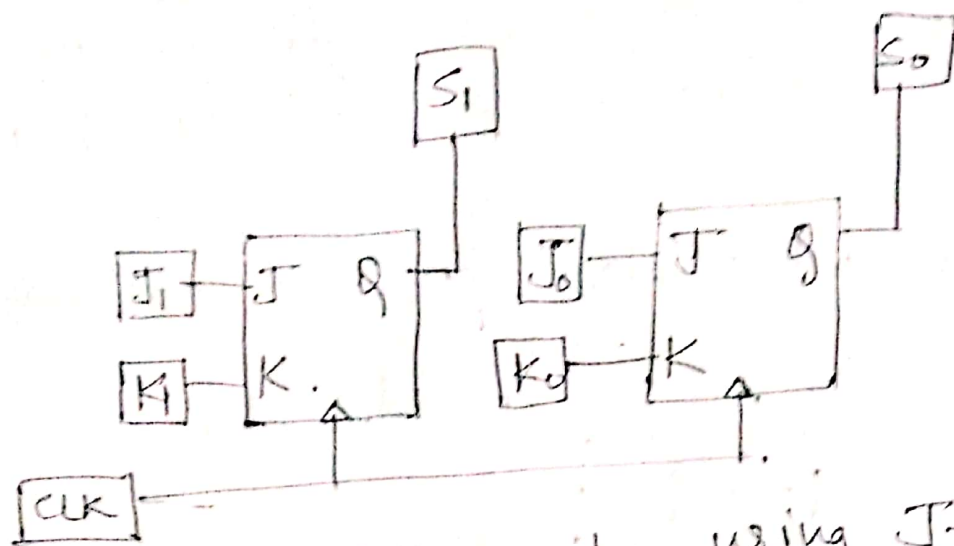


Fig. 2-bit counter using J-K flipflop.

Q.2) Design 8-bit adder using a single bit full-adder and shift register.
 A, B (Inputs) Y (output).


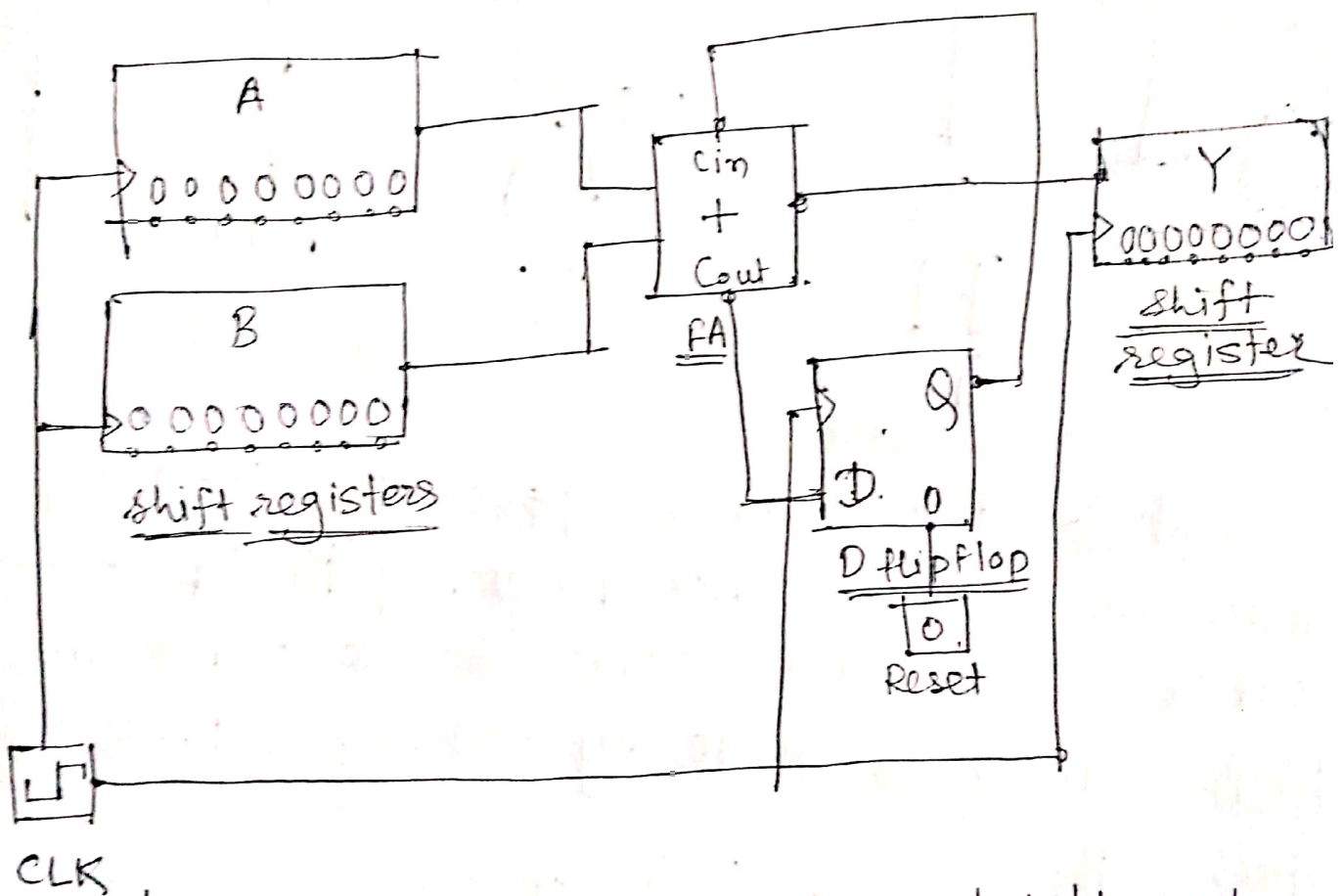


Fig. 8-bit FA using 1-bit FA and shift registers.

It will require 8 clock pulses for complete addition i.e. $Y = A + B$. If we use a FA which is capa

ble of adding more no. of bits, then consequently no. of clock pulses (time) req. will reduce proportionately.

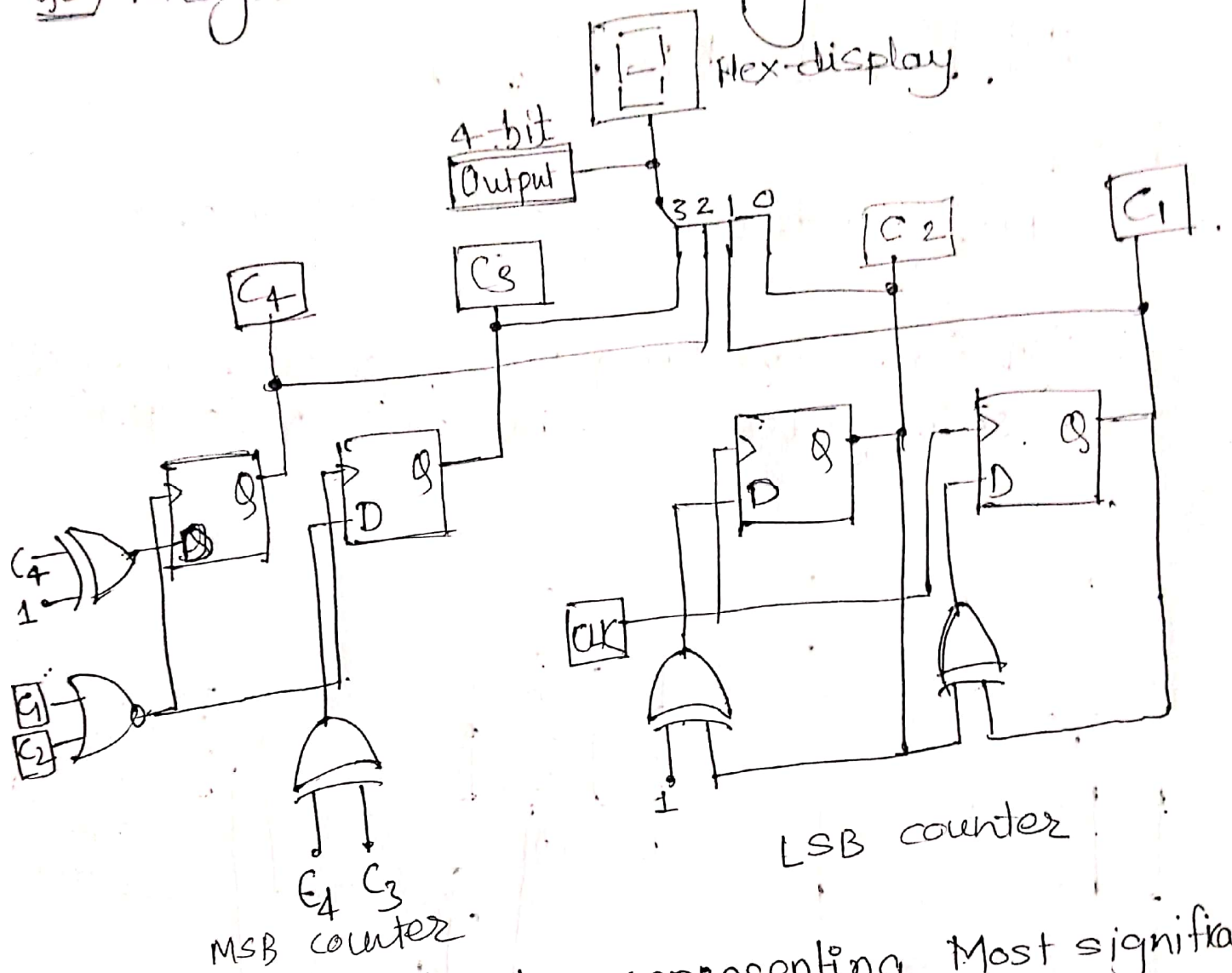Q.3) Design a 4-bit counter using two 2-bit counters.



Just for the counter representing Most significant bits we have to reduce frequency to $1/4$ of the other. This can be done if clock for the MSB counter is made by taking a NOR of two LSBs.

